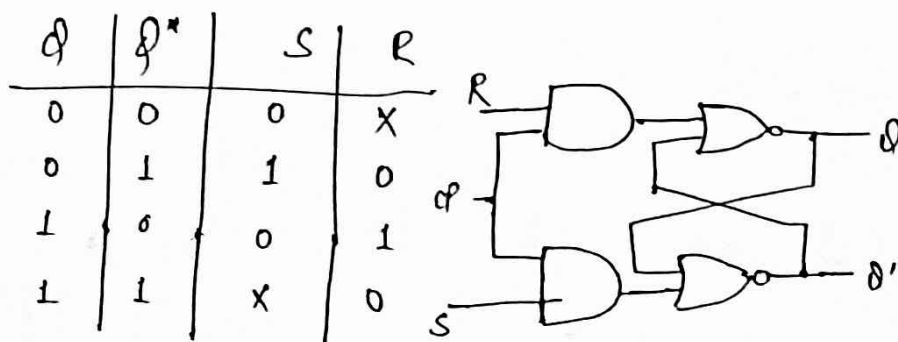


Aim:- Verify the excitation table of various FLIP-FLOPS.


Theory:- Flip-flops are synchronous bi-stable device. The term Synchronous means the output changes state only when the clock input is triggered. That is changes in the output occur in synchronization with the clock. A flip-flop circuit has two ~~input~~ outputs, one for the ~~normal~~ normal value and one for the complement value of the stored bit. Since memory elements in sequential circuits are usually flip-flops, it is worth summarizing the behaviour of various flip-flops types before proceeding further. All flip-flops can be divided into four basic types:- SR, JK, D and T.

Excitation Table:-

SR Flip-flop:-




JK Flip Flop:-

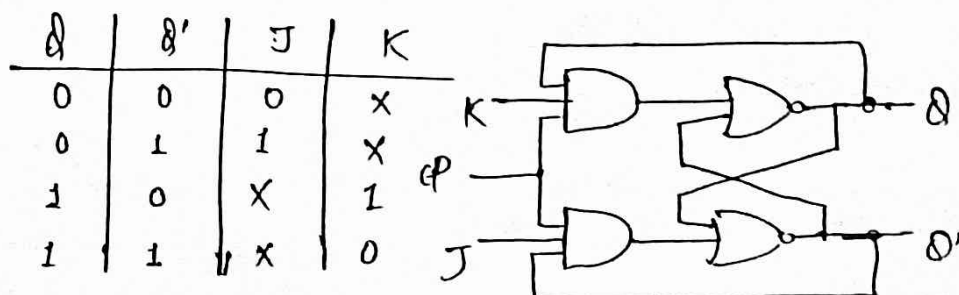

D-Flip Flop

Q	Q^*	D
0	0	0
0	1	1
1	0	0
1	1	1

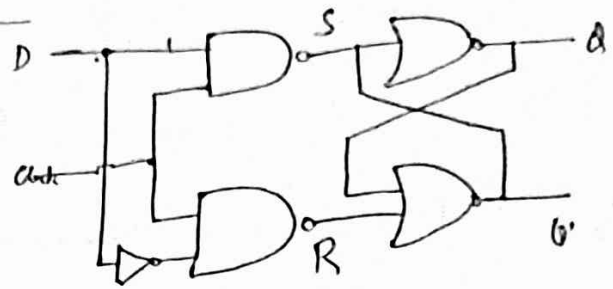

T-Flip Flop

Q	Q^*	T
0	0	0
0	1	1
1	0	1
1	1	0

